
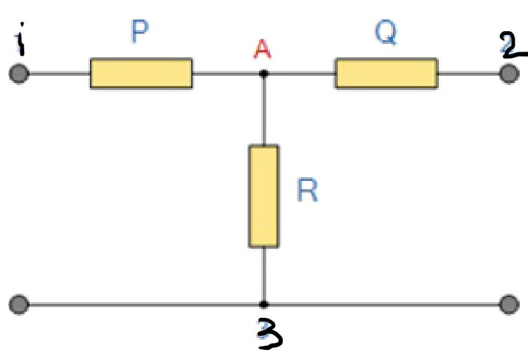


Star - Delta Network

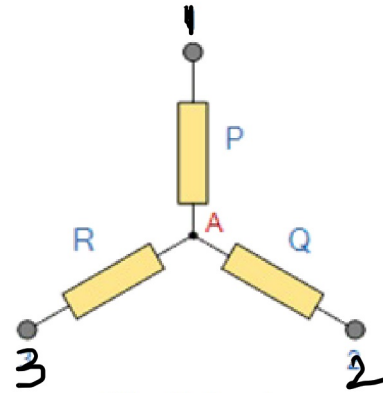


T-Network




Star-Network

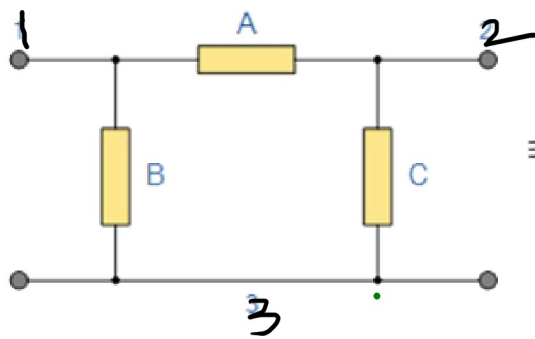A resistive network consisting of three impedances can be connected together to form a T or "Tee" Star or Y type network.




Pi-Network

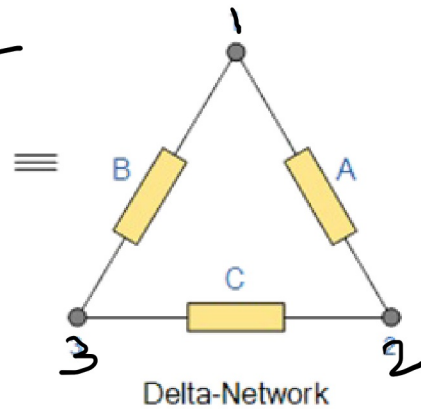

Delta-Network

Pi or π type resistor network or Delta or Δ type network

Delta- Star Transformation

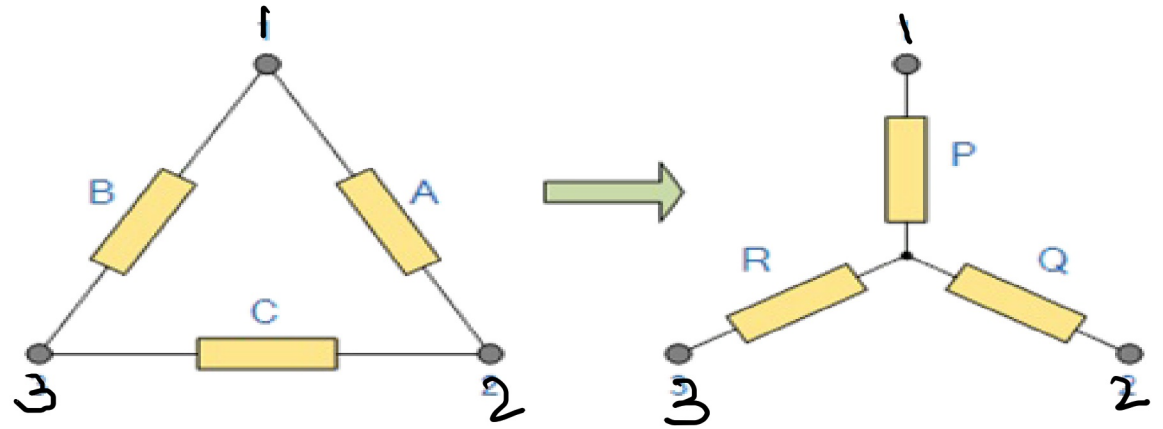

Resistances between terminals 1 and 2.

$$A \parallel (B+C) = P+Q$$

$$\frac{A(B+C)}{A+B+C} = P+Q \quad \text{--- (i)}$$

Resistances between terminals 2 and 3.

$$C \parallel (A+B) = Q+R \quad \text{---}$$

$$\frac{C(A+B)}{A+B+C} = Q+R \quad \text{--- (ii)}$$

Resistances between terminals 3 and 1.

$$B \parallel (A+C) = P+R$$

$$\frac{B(A+C)}{A+B+C} = P+R \quad \text{--- (iii)}$$

Delta-Star Transformation

$$A || (B+C) = P+Q$$

$$\frac{A(B+C)}{A+B+C} = P+Q \text{ --- (i)}$$

$$C || (A+B) = Q+R \text{ ---}$$

$$\frac{C(A+B)}{A+B+C} = Q+R \text{ --- (ii)}$$

$$B || (A+C) = P+R$$

$$\frac{B(A+C)}{A+B+C} = P+R \text{ --- (iii)}$$

Adding (i) & (ii) & subtract (iii)

$$eq^n(i) + eq^n(ii) - eq^n(iii)$$

$$\frac{\cancel{AB} + \cancel{AC} + \cancel{AC} + \cancel{BC} - \cancel{AB} - \cancel{BC}}{A+B+C} = \cancel{P+Q} + \cancel{Q+R} - \cancel{P+R}$$

$$\frac{2AC}{A+B+C} = 2Q$$

$$Q = \frac{AC}{A+B+C}$$

$$eq^n(i) + eq^n(iii) - eq^n(ii)$$

$$\frac{\cancel{AB} + \cancel{AC} + \cancel{AB} + \cancel{BC} - \cancel{AC} - \cancel{BC}}{A+B+C} = \cancel{P+Q} + \cancel{P+R} - \cancel{Q+R}$$

$$\frac{2AB}{A+B+C} = 2P \quad \therefore P = \frac{AB}{A+B+C}$$

Similarly $R = \frac{BC}{A+B+C}$

Star-delta Transformation

$$P = \frac{AB}{A+B+C}$$

$$Q = \frac{AC}{A+B+C}$$

$$R = \frac{BC}{A+B+C}$$

$$PQ + QR + PR$$

$$PQ = \frac{A^2BC}{(A+B+C)^2}$$

$$QR = \frac{ABC^2}{(A+B+C)^2}$$

$$PR = \frac{AB^2C}{(A+B+C)^2}$$

$$PQ + QR + PR = \frac{A^2BC + ABC^2 + AB^2C}{(A+B+C)^2} = \frac{ABC(A+B+C)}{(A+B+C)^2}$$

$$PQ + QR + PR = \frac{ABC}{A+B+C}$$

$$\frac{PQ + QR + PR}{P} = \frac{\cancel{A}BC}{\cancel{(A+B+C)}} \times \frac{\cancel{(A+B+C)}}{\cancel{AB}} = C$$

$$C = \frac{PQ + QR + PR}{P}$$

Star-delta Transformation

$$P = \frac{AB}{A+B+C}$$

$$Q = \frac{AC}{A+B+C}$$

$$R = \frac{BC}{A+B+C}$$

$$PQ + QR + PR$$

$$PQ = \frac{A^2BC}{(A+B+C)^2}$$

$$QR = \frac{ABC^2}{(A+B+C)^2}$$

$$PR = \frac{AB^2C}{(A+B+C)^2}$$

$$PQ + QR + PR = \frac{A^2BC + ABC^2 + AB^2C}{(A+B+C)^2} = \frac{ABC(A+B+C)}{(A+B+C)^2}$$

$$PQ + QR + PR = \frac{ABC}{A+B+C}$$

$$\frac{PQ + QR + PR}{Q} = \frac{ABC}{(A+B+C)} \times \frac{(A+B+C)}{AC}$$

$$B = \frac{PQ + QR + PR}{Q}$$

Star-delta Transformation

$$P = \frac{AB}{A+B+C}$$

$$Q = \frac{AC}{A+B+C}$$

$$R = \frac{BC}{A+B+C}$$

$$PQ + QR + PR$$

$$PQ = \frac{A^2BC}{(A+B+C)^2}$$

$$QR = \frac{ABC^2}{(A+B+C)^2}$$

$$PR = \frac{AB^2C}{(A+B+C)^2}$$

$$PQ + QR + PR = \frac{A^2BC + ABC^2 + AB^2C}{(A+B+C)^2} = \frac{ABC(A+B+C)}{(A+B+C)^2}$$

$$PQ + QR + PR = \frac{ABC}{A+B+C}$$

$$\frac{PQ + QR + PR}{Q} = \frac{ABC}{(A+B+C)} \times \frac{(A+B+C)}{AC}$$

$$B = \frac{PQ + QR + PR}{Q}$$

Star-delta Transformation

$$P = \frac{AB}{A+B+C}$$

$$Q = \frac{AC}{A+B+C}$$

$$R = \frac{BC}{A+B+C}$$

$$PQ + QR + PR$$

$$PQ = \frac{A^2 BC}{(A+B+C)^2}$$

$$QR = \frac{ABC^2}{(A+B+C)^2}$$

$$PR = \frac{AB^2 C}{(A+B+C)^2}$$


$$PQ + QR + PR = \frac{A^2 BC + ABC^2 + AB^2 C}{(A+B+C)^2} = \frac{ABC(A+B+C)}{(A+B+C)^2}$$

$$PQ + QR + PR = \frac{ABC}{A+B+C}$$

$$\frac{PQ + QR + PR}{R} = \frac{ABC}{A+B+C} \times \frac{A+B+C}{BC}$$

$$A = \frac{PQ + QR + PR}{R}$$

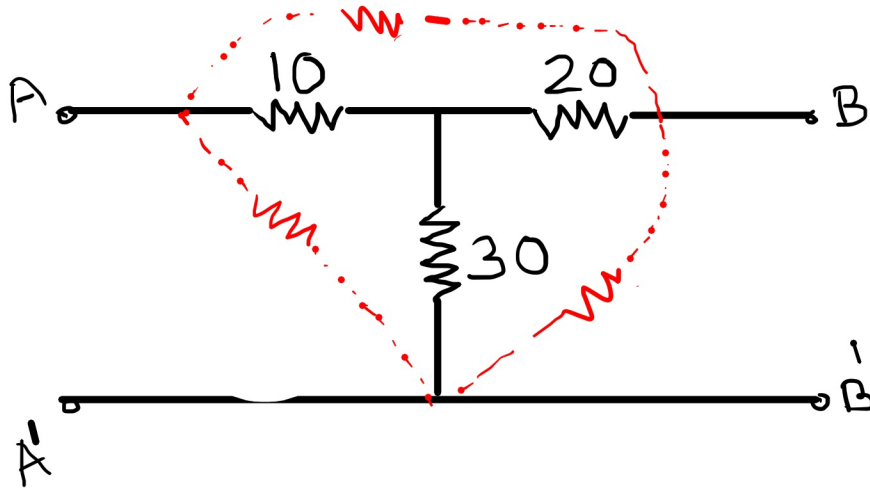Example:1 Convert following star networks into equivalent delta network





$$PQ + QR + PR = 10 \times 20 + 20 \times 30 + 30 \times 10$$

$$PQ + QR + PR = 200 + 600 + 300 = 1100$$

$$A = \frac{1100}{20} = 55 \Omega$$

$$B = \frac{1100}{30} = \frac{110}{3} = 36.66 \Omega$$

$$C = \frac{1100}{10} = 110 \Omega$$

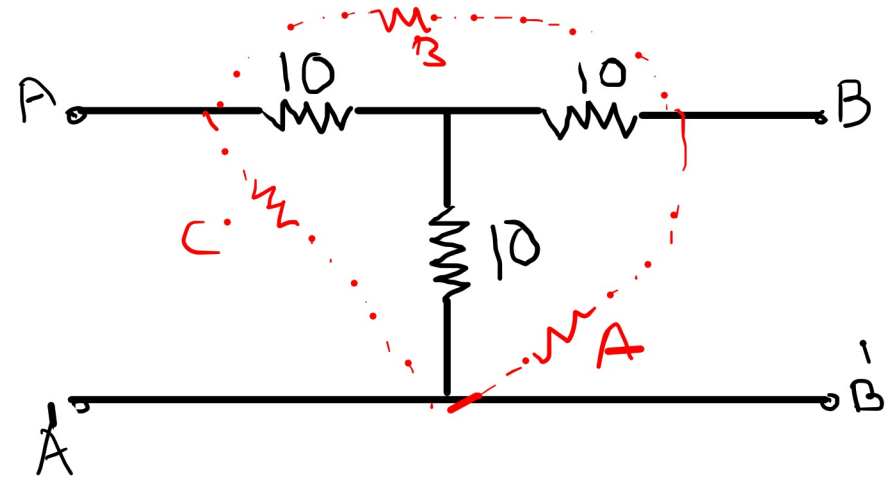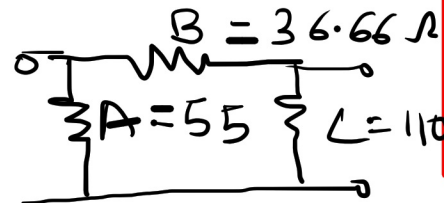


$$A = \frac{10 \times 10 + 10 \times 10 + 10 \times 10}{10}$$

$$A = \frac{300}{10} = 30 \Omega$$

$$A = B = C = 30 \Omega$$

Star-Delta Transformation

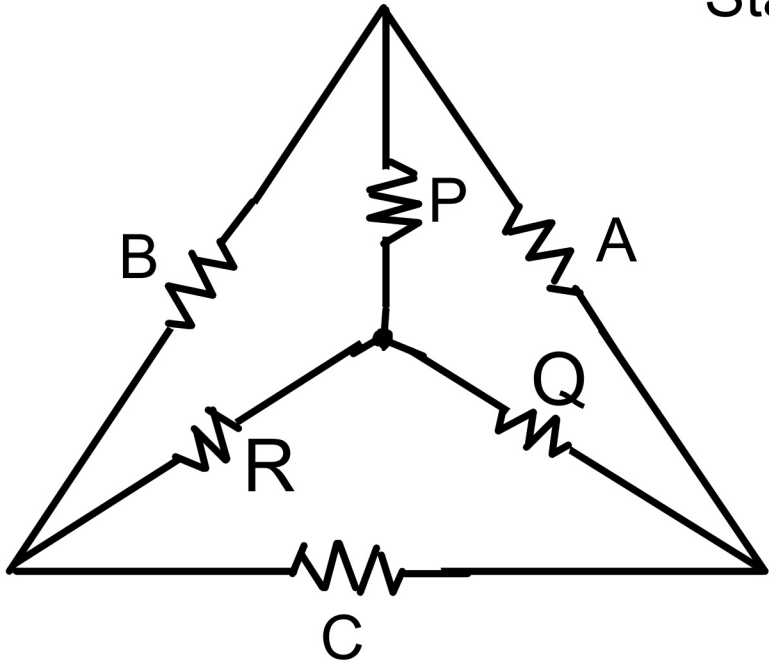

Delta - Star

$$P = \frac{AB}{A+B+C}, \quad Q = \frac{AC}{A+B+C}$$

$$R = \frac{BC}{A+B+C}$$

Star - Delta



$$A = \frac{PQ + QR + PR}{R}$$

$$B = \frac{PQ + QR + PR}{Q}$$

$$C = \frac{PQ + QR + PR}{P}$$

$$\underline{Z_R = PQ + QR + PR}$$

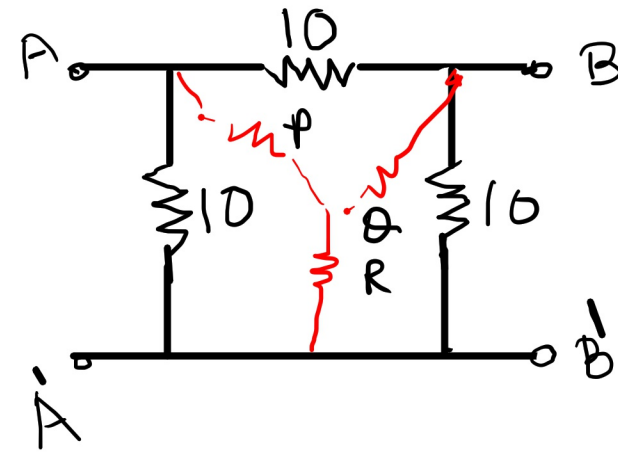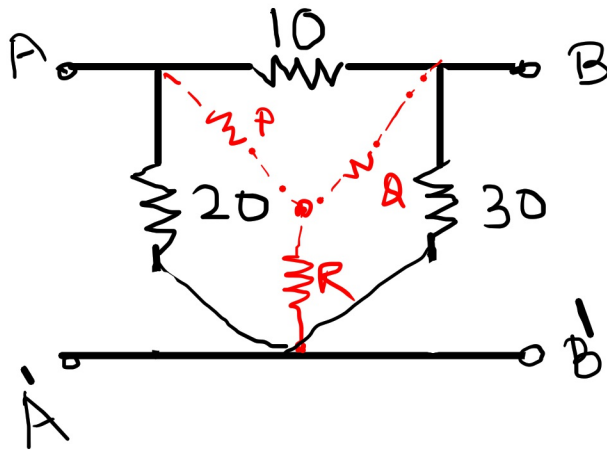Example:2 Convert following delta networks into equivalent star network



$$P = \frac{10 \times 20}{10 + 20 + 30} = \frac{200}{60} = \frac{20}{6} \Omega$$



$$Q = \frac{10 \times 30}{10 + 20 + 30} = \frac{300}{60} = 5 \Omega$$

$$R = \frac{20 \times 30}{10 + 20 + 30} = \frac{600}{60} = 10 \Omega$$

$$P = Q = R = \frac{10 \times 10}{10 + 10 + 10} = \frac{100}{30} = 3.33 \Omega$$




Star-Delta Transformation.

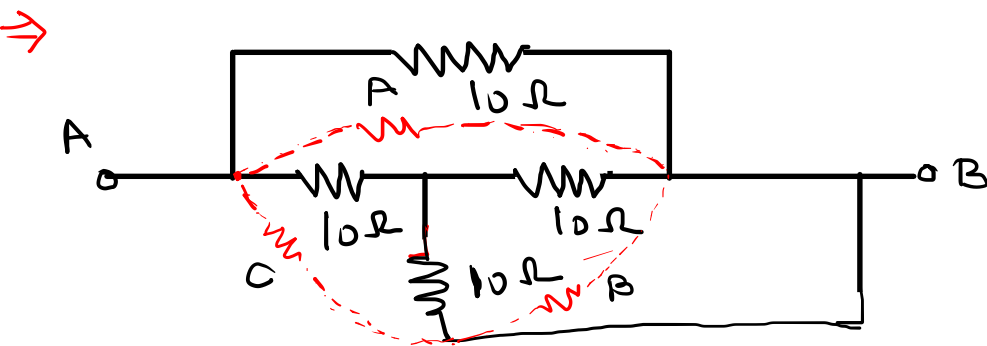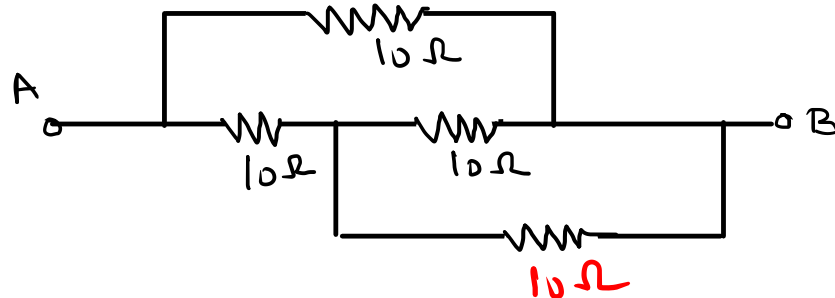Ex. ① Find Resistance between terminals A and B.



$$A = B = C = \frac{10 \times 10 + 10 \times 10 + 10 \times 10}{10}$$


$$= \frac{300}{10} = 30 \Omega$$

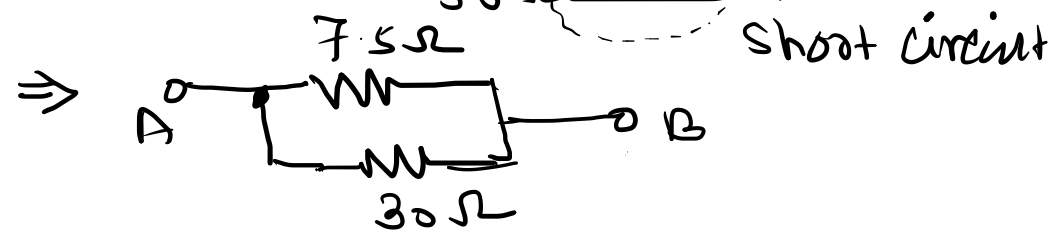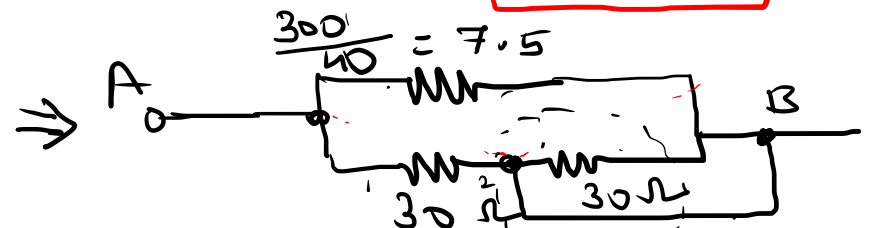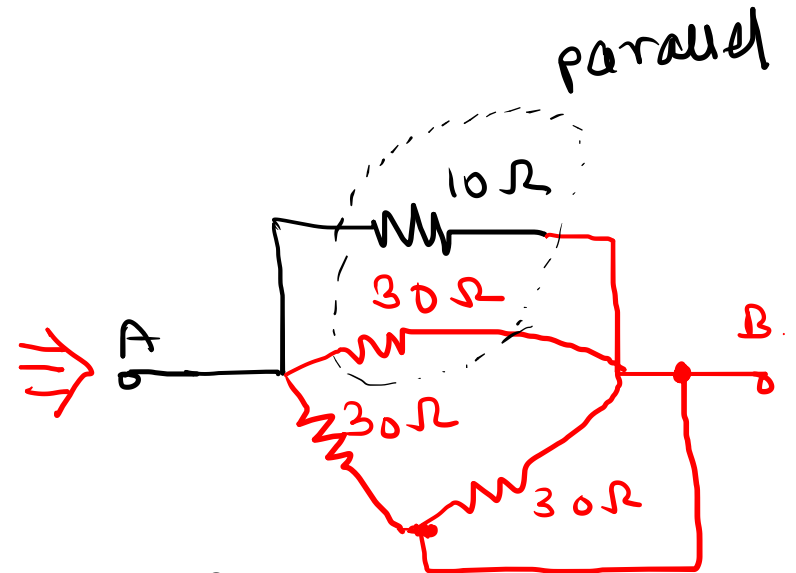


$$R_{AB} = \frac{7.5 \times 30}{7.5 + 30} = 6 \Omega$$

Star-Delta Transformation.

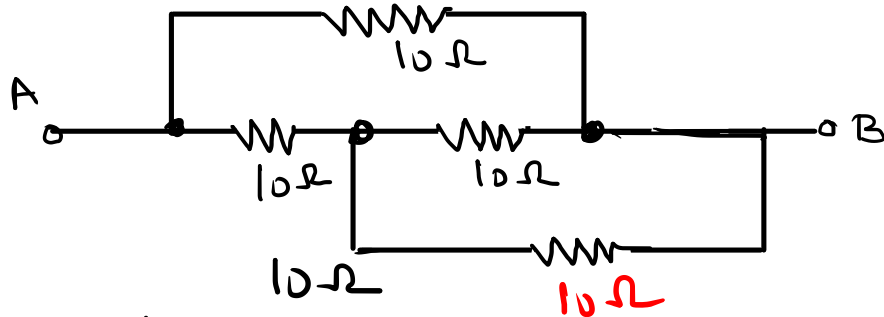Ex. ① Find Resistance between terminals A and B.




⇒

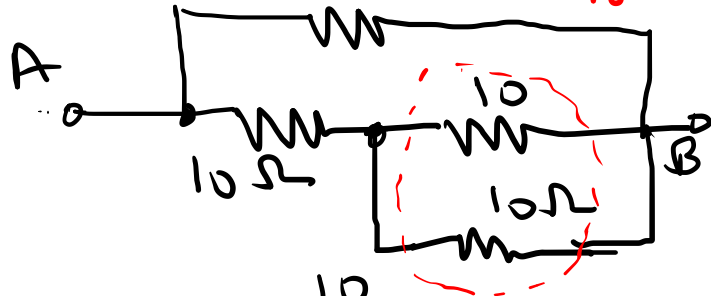


$$R_{AB} = \frac{10 \times 15}{10 + 15} = \frac{150}{25}$$

$$R_{AB} = 6 \Omega$$

⇒


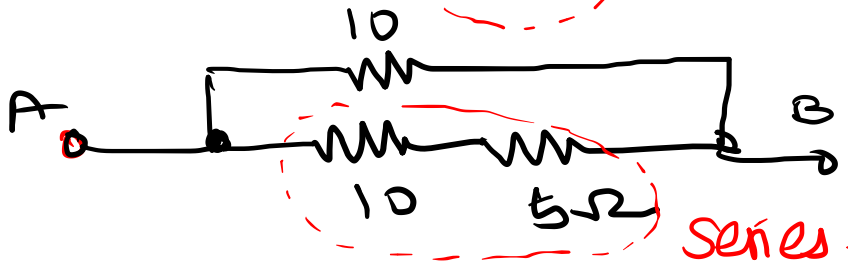


⇒

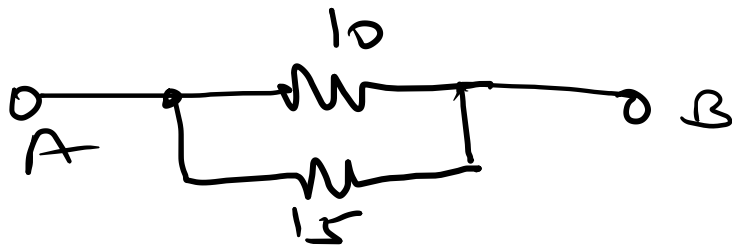


Ex. 11


Find R_{AB} $10\ \Omega$

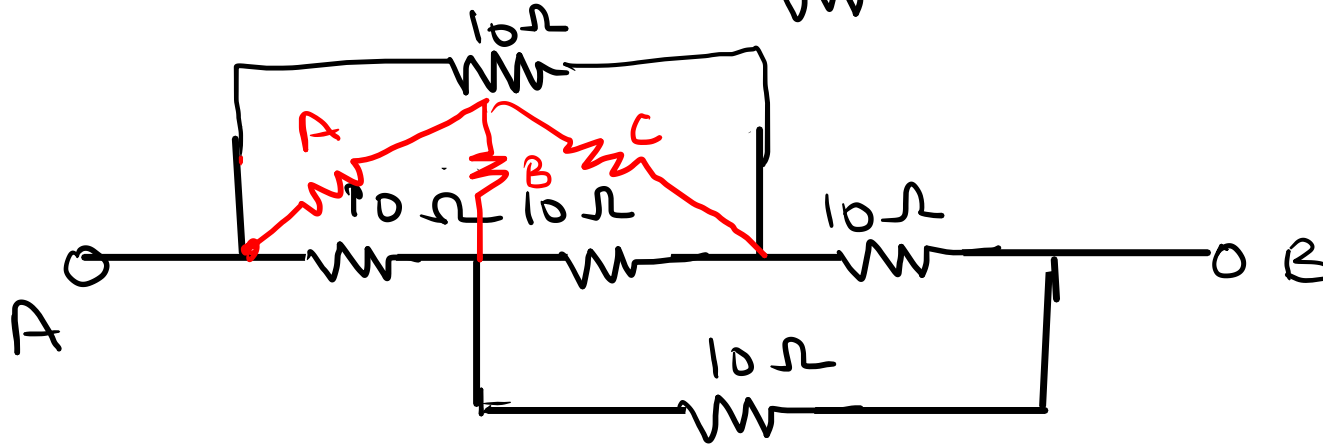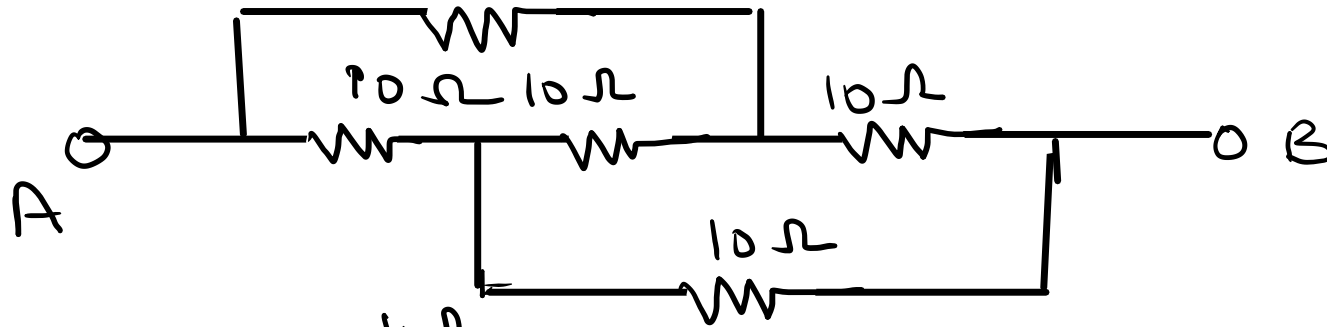
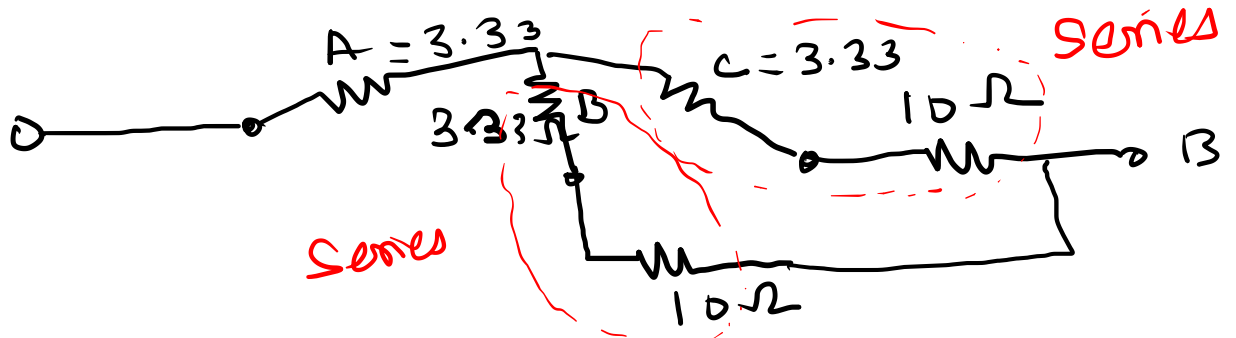
$$A = B = C = \frac{10 \times 10}{10 + 10 + 10} = \frac{100}{30} = 3.33\ \Omega$$




Parallel

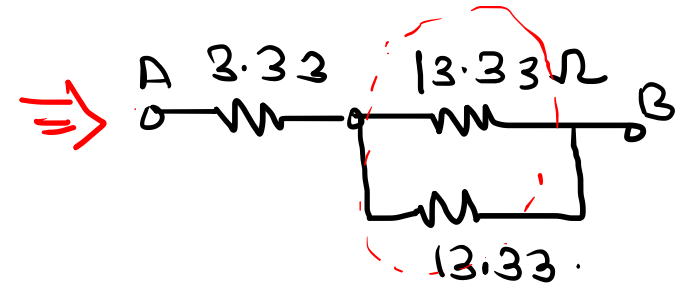


$$R_{AB} = 3.33 + 6.66 = 9.99 \approx 10\ \Omega$$

Star-Delta Transformation

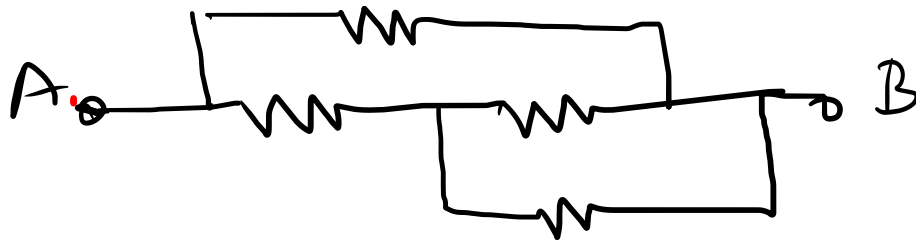


$$\Rightarrow 13.33 \parallel 3.33$$

$$2.66 \Omega$$

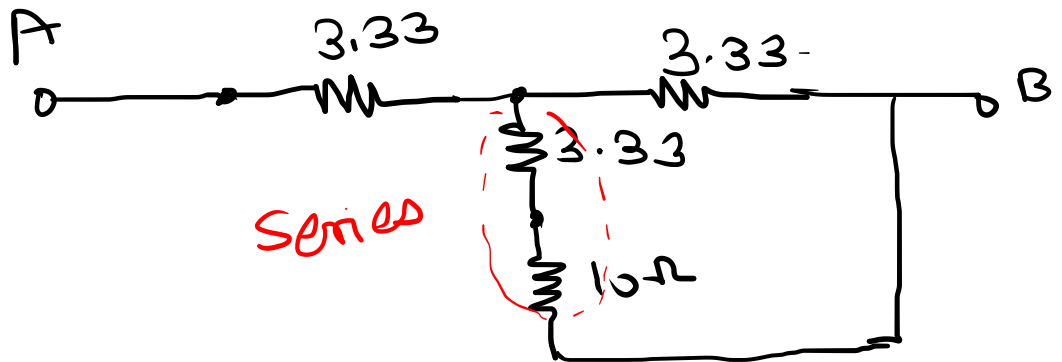


Series

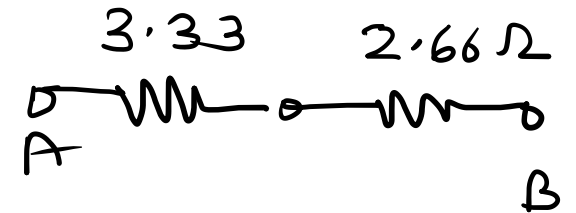

$$R_{AB} = 3.33 + 2.66$$



$$R_{AB} = 5.99 \approx 6 \Omega$$

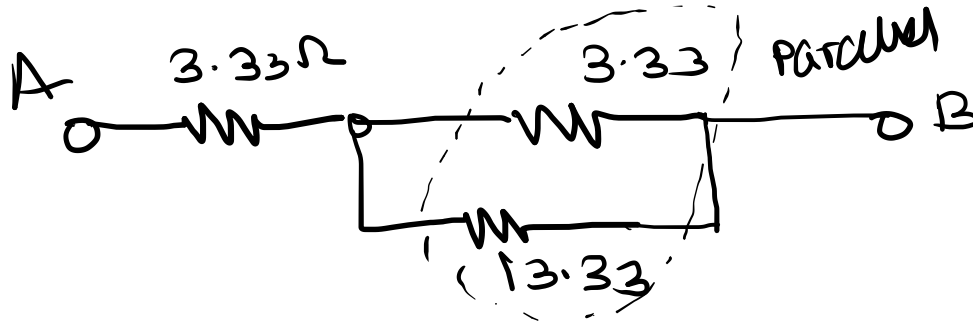

Parallel

Star-Delta Transformation.


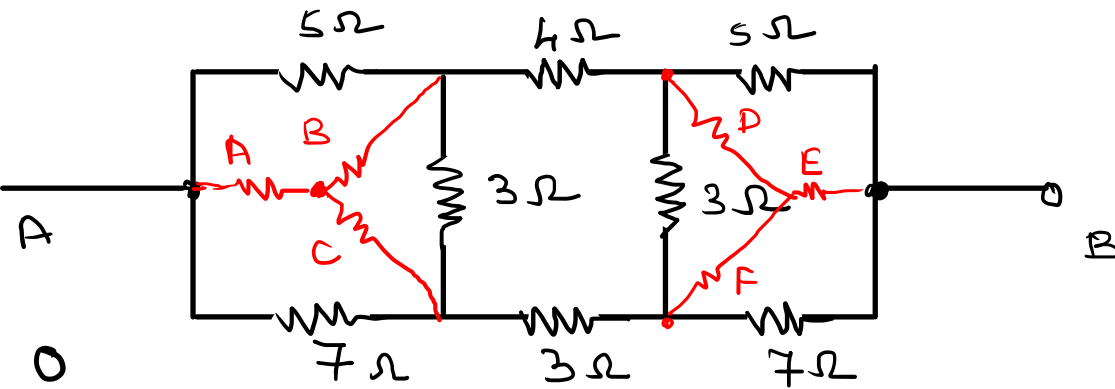
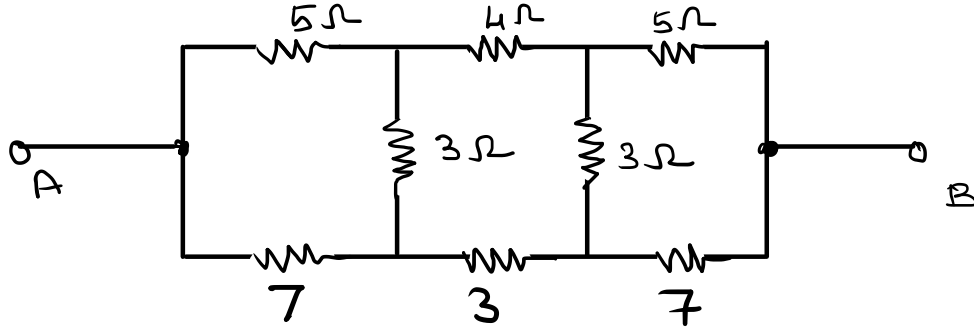
Ex. 11 Find Resistance between terminals A and B.



$$A = \frac{7 \times 5}{7 + 3 + 5} = \frac{35}{15} = 2.33 \Omega \quad B = \frac{5 \times 3}{15} = 1 \Omega$$


$$D = \frac{15}{15} = 1 \Omega, \quad E = \frac{35}{15} = 2.33 \Omega, \quad F = \frac{21}{15} = 1.4 \Omega$$

$$C = \frac{21}{15} = 1.4 \Omega$$

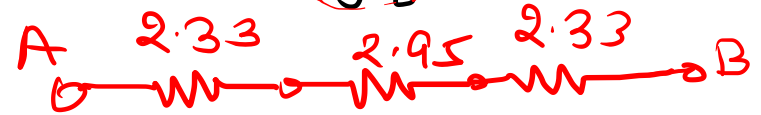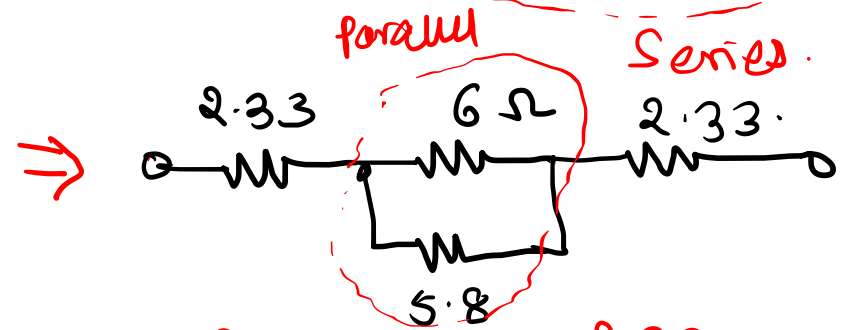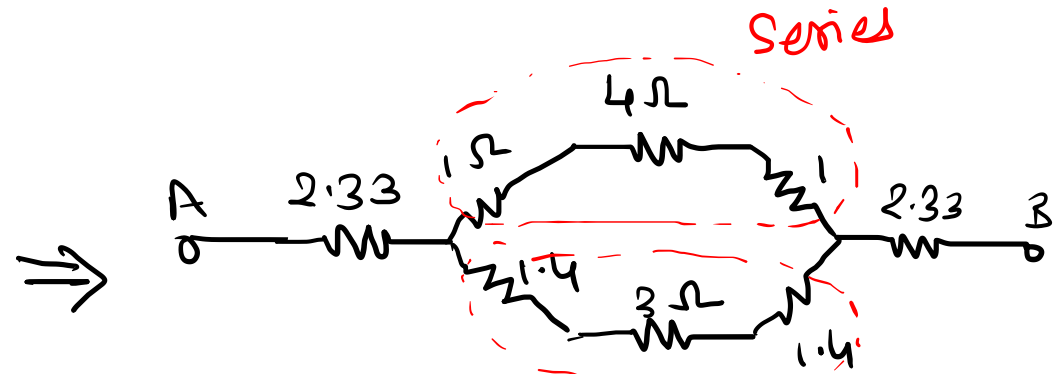



$$R_{AB} = 7.61 \Omega$$

Star-Delta Transformation

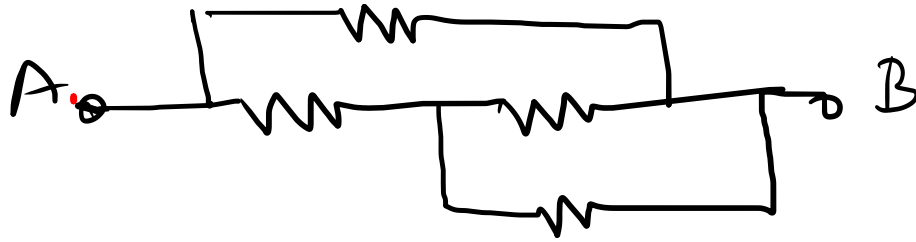


$$\Rightarrow 13.33 \parallel 3.33$$

$$2.66 \Omega$$

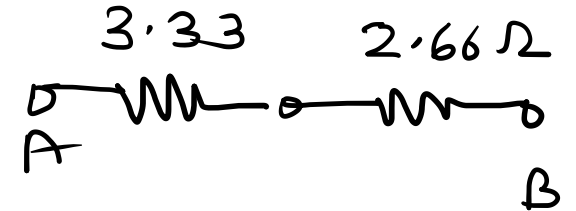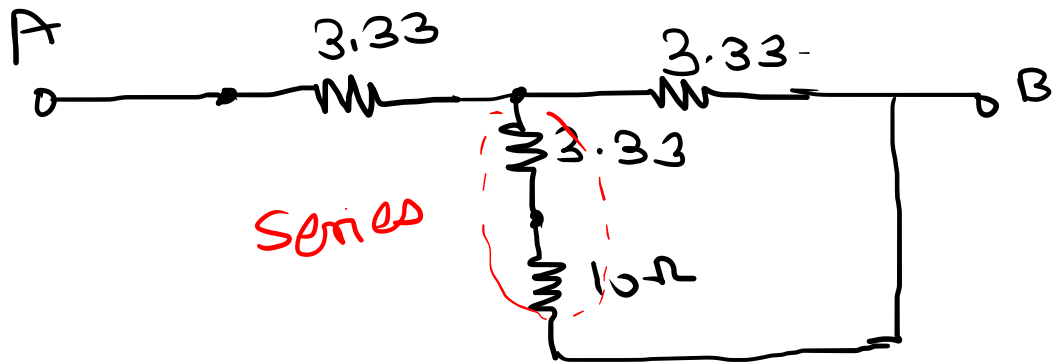


$$R_{AB} = 3.33 + 2.66$$

$$R_{AB} = 5.99 \approx 6 \Omega$$

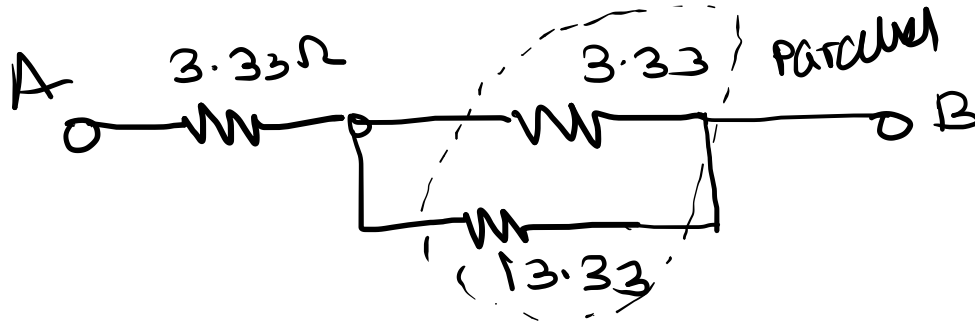


⇒ Numericals Based on Kirchoff's Laws.

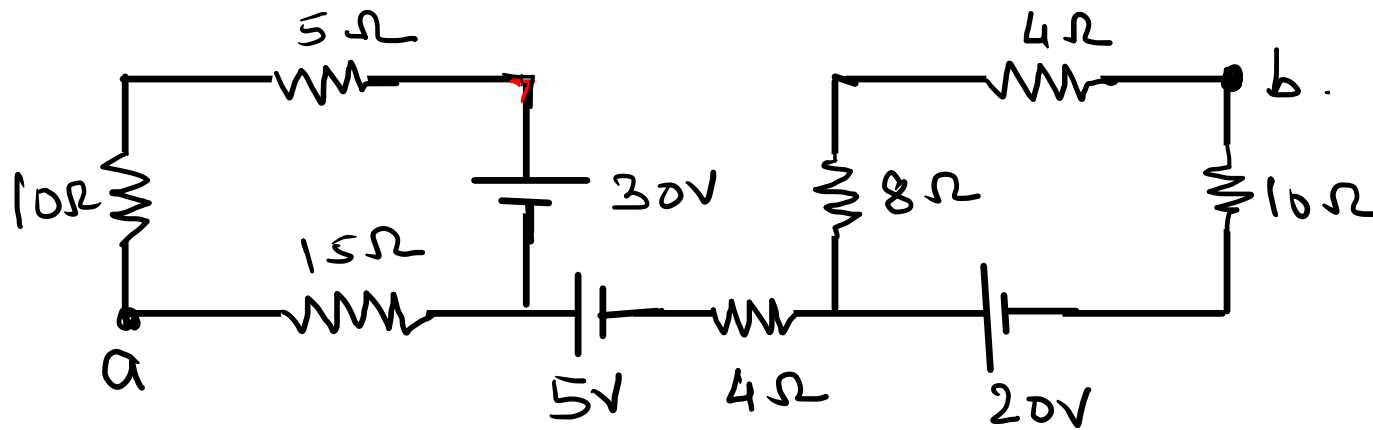① Find voltage between terminals a and b.



⇒

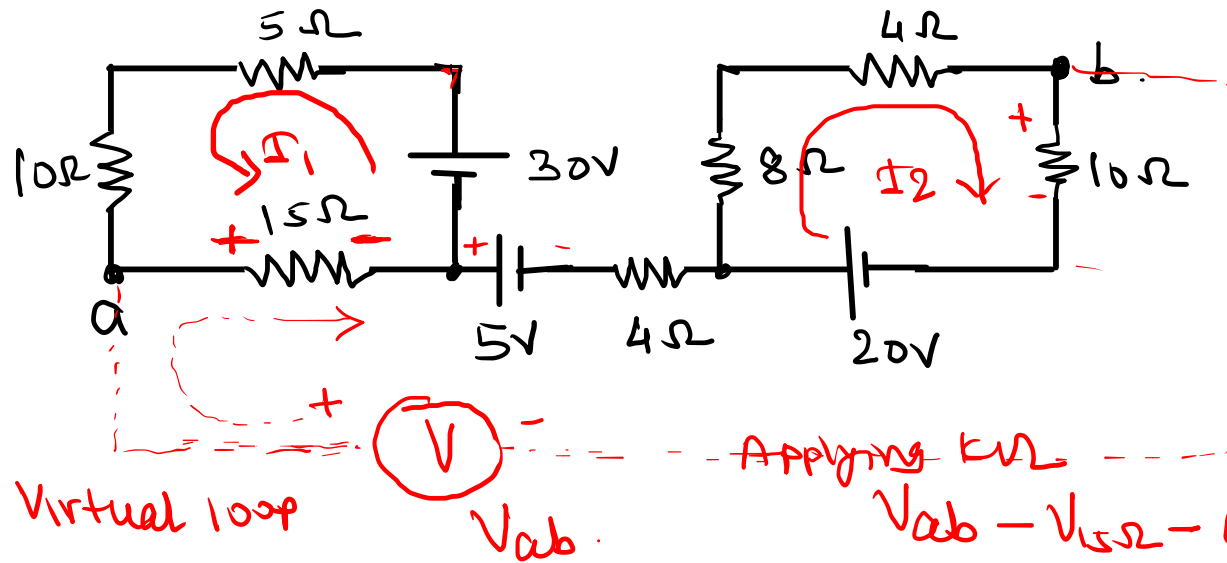

$$I_1 = \frac{30}{5 + 10 + 15} = 1A$$

$$I_2 = \frac{20}{8 + 4 + 10} = \frac{20}{22} = 0.9A$$

Virtual loop

V
V_{ab}

Applying KVL

$$V_{ab} - V_{15\Omega} - (5V) - V_{4\Omega} - 20 - V_{10\Omega} = 0$$



$$V_{ab} - (15 \times 1) - 5 - 0 - 20 + (10 \times 0.9) = 0$$

$$V_{ab} - 15 - 5 - 20 + 9 = 0$$

$$V_{ab} = 31V$$

⇒ Numericals Based on Kirchoff's Laws.

① Find voltage V_{AB} .

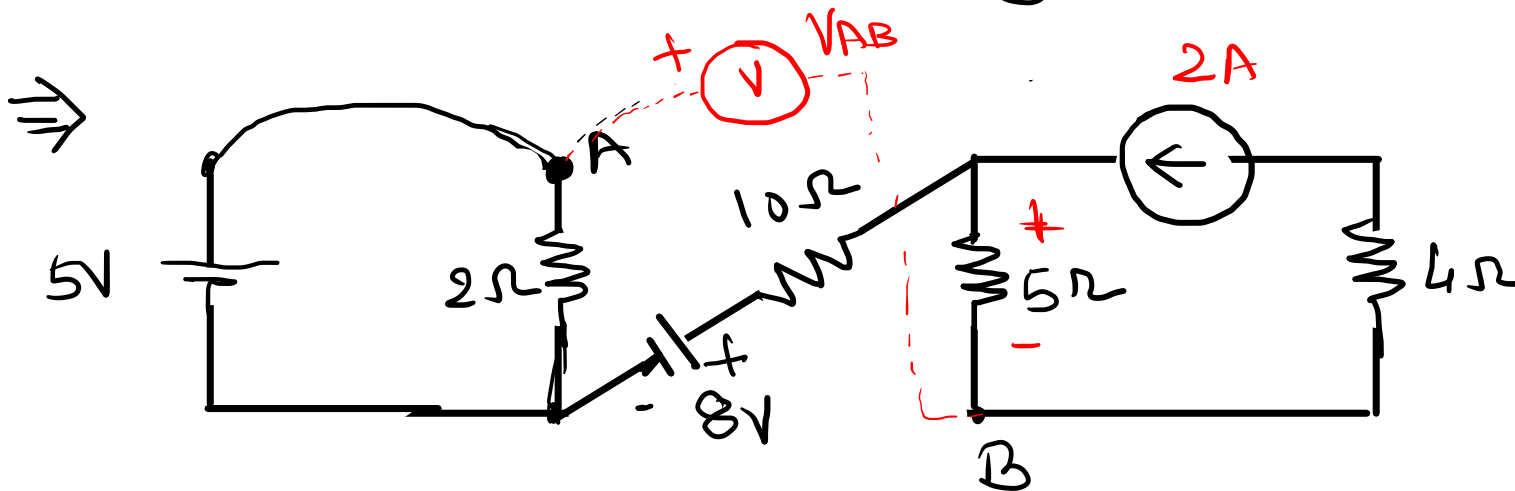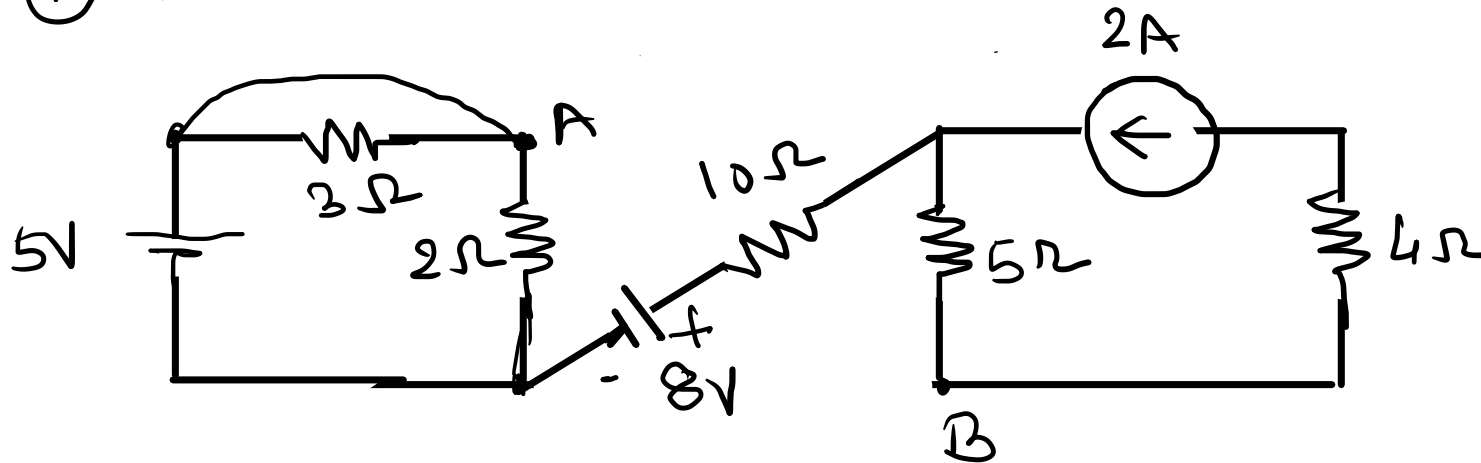

Applying KVL



$$V_{AB} - V_{2\Omega} + 8 + V_{10\Omega} - V_{5\Omega} = 0$$

$$V_{AB} - 5 + 8 + 0 - 10 = 0$$

$$\boxed{V_{AB} = 7V}$$

⇒ Numericals Based on Kirchoff's Laws.

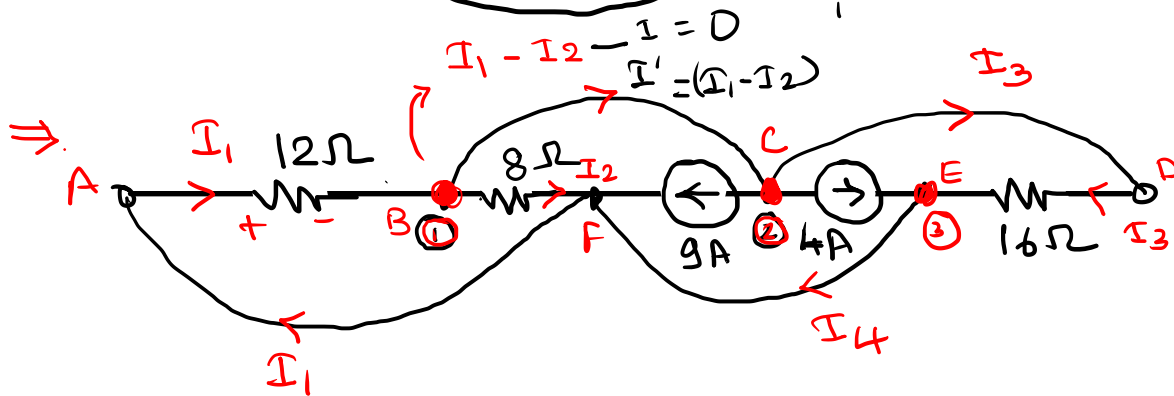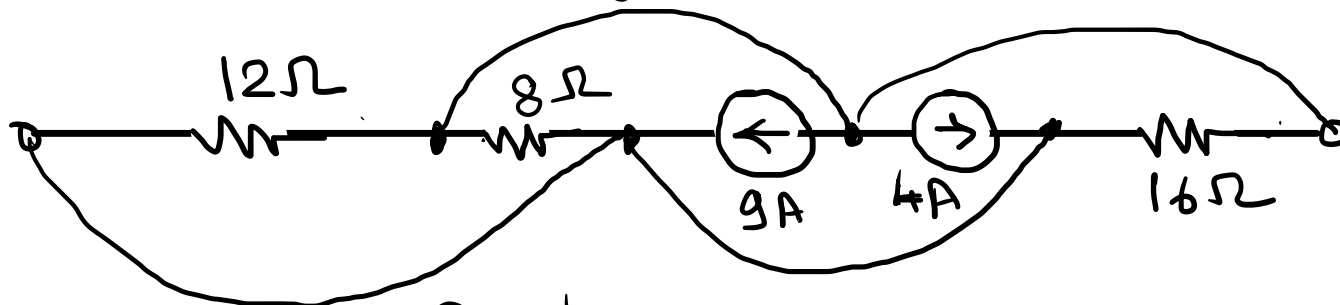(iii) Find current through 12Ω & 16Ω resistors.



KVL at node (2)

$$(I_1 - I_2) - 9 - 4 - I_3 = 0$$

$$I_3 = (I_1 - I_2) - 13 \quad \text{--- (1)}$$

KVL at node (3)

$$I_4 = I_3 + 4 \quad \text{--- (2)}$$

KVL to closed path (A-B-F-A)

$$-12I_1 - 8I_2 = 0$$

$$3I_1 + 2I_2 = 0 \quad \text{--- (3) } \checkmark$$

From equation (1) $I_1 - I_2 - I_3 = 13 \quad \text{--- (5)}$

Solving (3), (4) and (5)

KVL to closed path

(A-B-C-D-E-F-A)

$$-12I_1 - 16I_3 = 0$$

$$3I_1 + 4I_3 = 0 \quad \text{--- (4)}$$

$$I_1 = 4A (\rightarrow), \quad I_2 = -6A$$

$$I_3 = -3A (\leftarrow)$$